

Forelesning 06: Regular Sequential Circuits

Hieu Nguyen

Innold

- Konstruerer Mod-M teller ved bruk **synkron metode**
- Simulerer Mod-M teller
- Tester **Mod-16** teller i Basys-3 ved bruk **hex2seg krets**

Design 05: Mod-M teller

- **Mod-M** teller er en krets som øker sin verdi 1 om gangen og starter fra **0** til **M-1** og hopper rundt (wraps around).
- For eksempel: Mod-10 teller skal telle 0, 1, 2, 3, 4, 5, 6, 7, 8, **9, 0**, 1....
- **Mod-M** teller bør ha to **generics**
 - **M**: spesifiserer tellerbegrensning
 - **N**: spesifiserer antall nødvendige biter i state register. **$N = \log_2(M)$**
 - **Eksempel**: Hvis en konstruerer Mod-16 teller. Dette betyr at **M = 16**, og telleren har 16 tilstander i intern minne. Derfor, trenger vi **N = 4** D-FF stykker for å lagre alle tilstander.

Design 05: Mod-M teller


- **Inngangssignaler**

- Clock signal - clk
- Reset signal - rst
- Enable signal – en

- **Utgangssignaler**


- Tellers verdi – q
- Max tick – max_tick

Entity Declaration

 

Design 05: Mod-M teller

State register

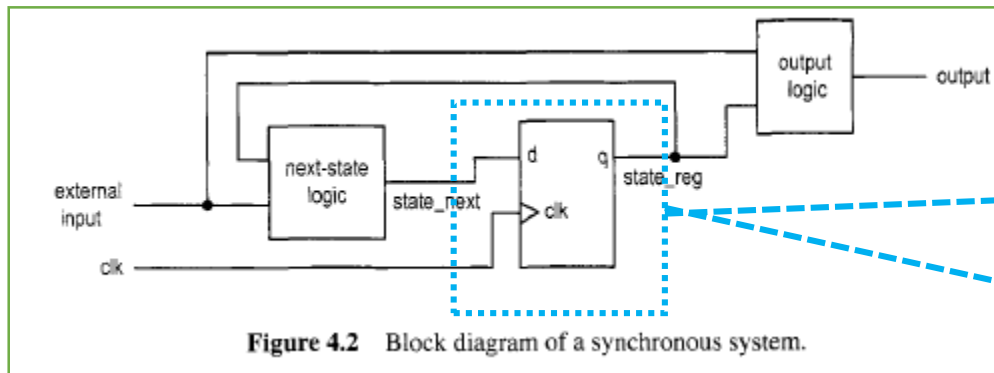


```
Listing 4.11
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity mod_m_counter is
    generic(
        N: integer := 4;      -- number of bits
        M: integer := 10     -- mod-M
    );
    port(
        clk, reset: in std_logic;
        max_tick: out std_logic;
        q: out std_logic_vector(N-1 downto 0)
    );
end mod_m_counter;

architecture arch of mod_m_counter is
    signal r_reg: unsigned(N-1 downto 0);
    signal r_next: unsigned(N-1 downto 0);
begin
    -- register
    process(clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;
    -- next-state logic
    r_next <= (others=>'0') when r_reg=(M-1) else
        r_reg + 1;
    -- output logic
    q <= std_logic_vector(r_reg);
    max_tick <= '1' when r_reg=(M-1) else '0';
end arch;
```

Design 05: Mod-M Teller

Next state logic

 

```
Listing 4.11
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity mod_m_counter is
    generic(
        N: integer := 4;    -- number of bits
        M: integer := 10    -- mod-M
    );
    port(
        clk, reset: in std_logic;
        max_tick: out std_logic;
        q: out std_logic_vector(N-1 downto 0)
    );
end mod_m_counter;


architecture arch of mod_m_counter is
    signal r_reg: unsigned(N-1 downto 0);
    signal r_next: unsigned(N-1 downto 0);
begin
    -- register
    process(clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;

    -- next-state logic
    r_next <= (others=>'0') when r_reg=(M-1) else
              r_reg + 1;

    -- output logic
    q <= std_logic_vector(r_reg);
    max_tick <= '1' when r_reg=(M-1) else '0';
end arch;
```

Design 05: Mod-M Teller


Output Logic

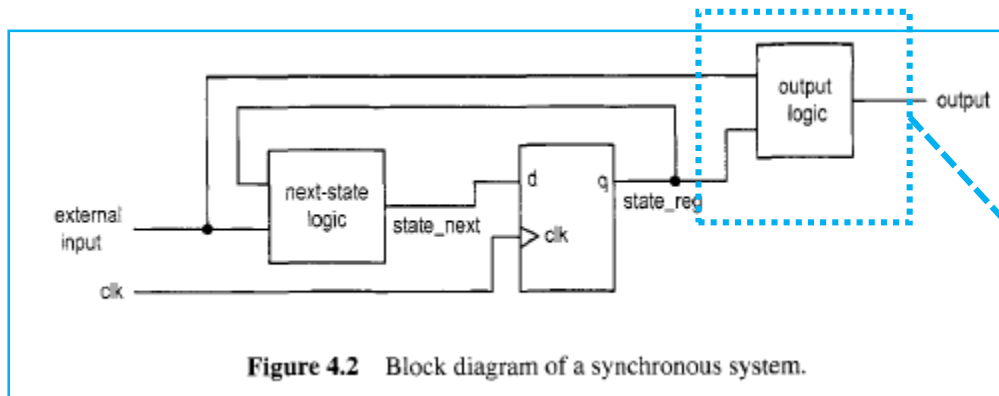


```
Listing 4.11
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;
entity mod_m_counter is
    generic(
        N: integer := 4;    -- number of bits
        M: integer := 10    -- mod-M
    );
    port(
        clk, reset: in std_logic;
        max_tick: out std_logic;
        q: out std_logic_vector(N-1 downto 0)
    );
end mod_m_counter;

architecture arch of mod_m_counter is
    signal r_reg: unsigned(N-1 downto 0);
    signal r_next: unsigned(N-1 downto 0);
begin
    -- register
    process(clk, reset)
    begin
        if (reset='1') then
            r_reg <= (others=>'0');
        elsif (clk'event and clk='1') then
            r_reg <= r_next;
        end if;
    end process;
    -- next-state logic
    r_next <= (others=>'0') when r_reg=(M-1) else
        r_reg + 1;
    -- output logic
    q <= std_logic_vector(r_reg);
    max_tick <= '1' when r_reg=(M-1) else '0';
end arch;
```

Test Bench – Test Mod-16 Counter

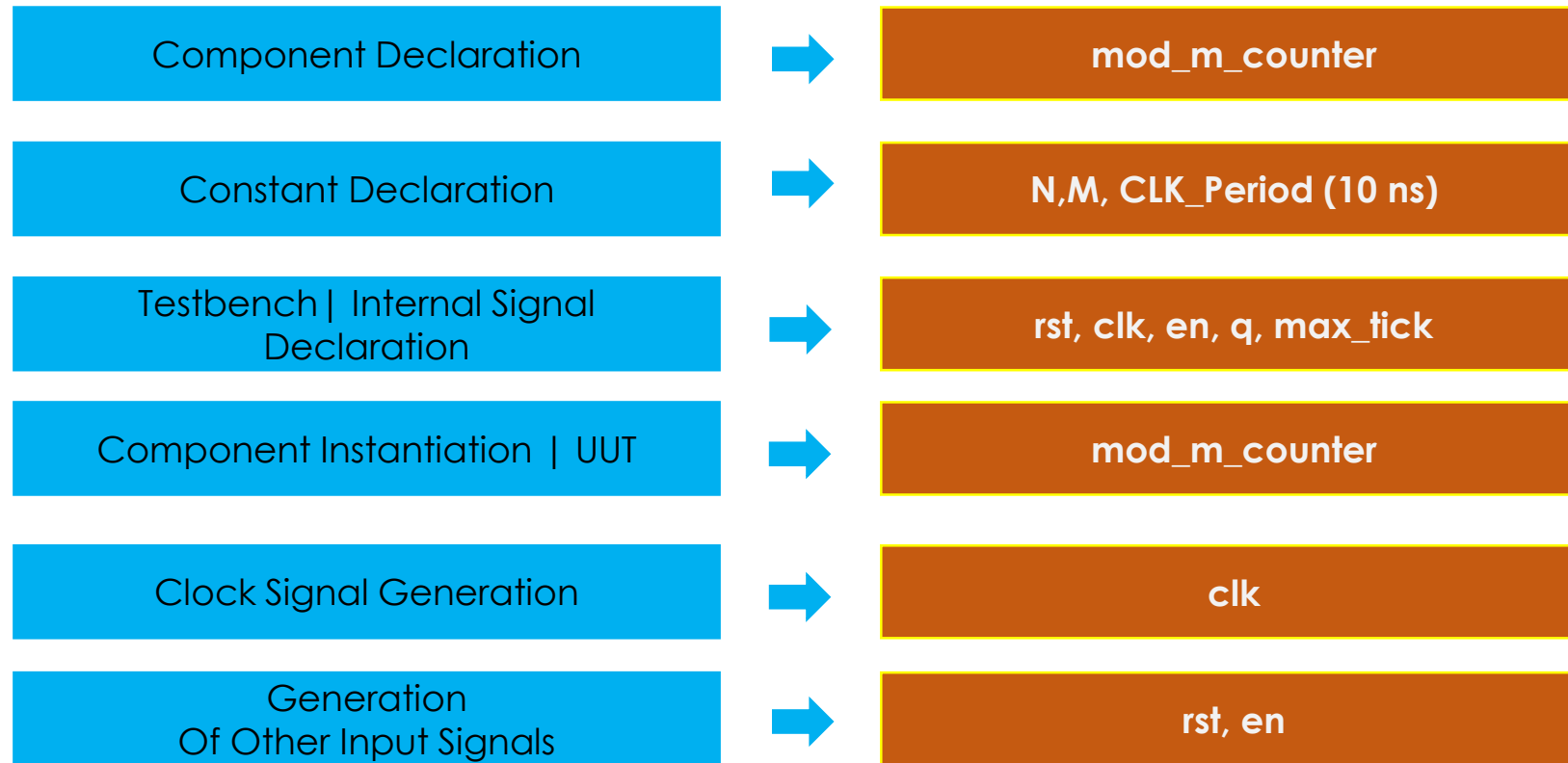


Mod-16 Counter | HardWare Testing (1)

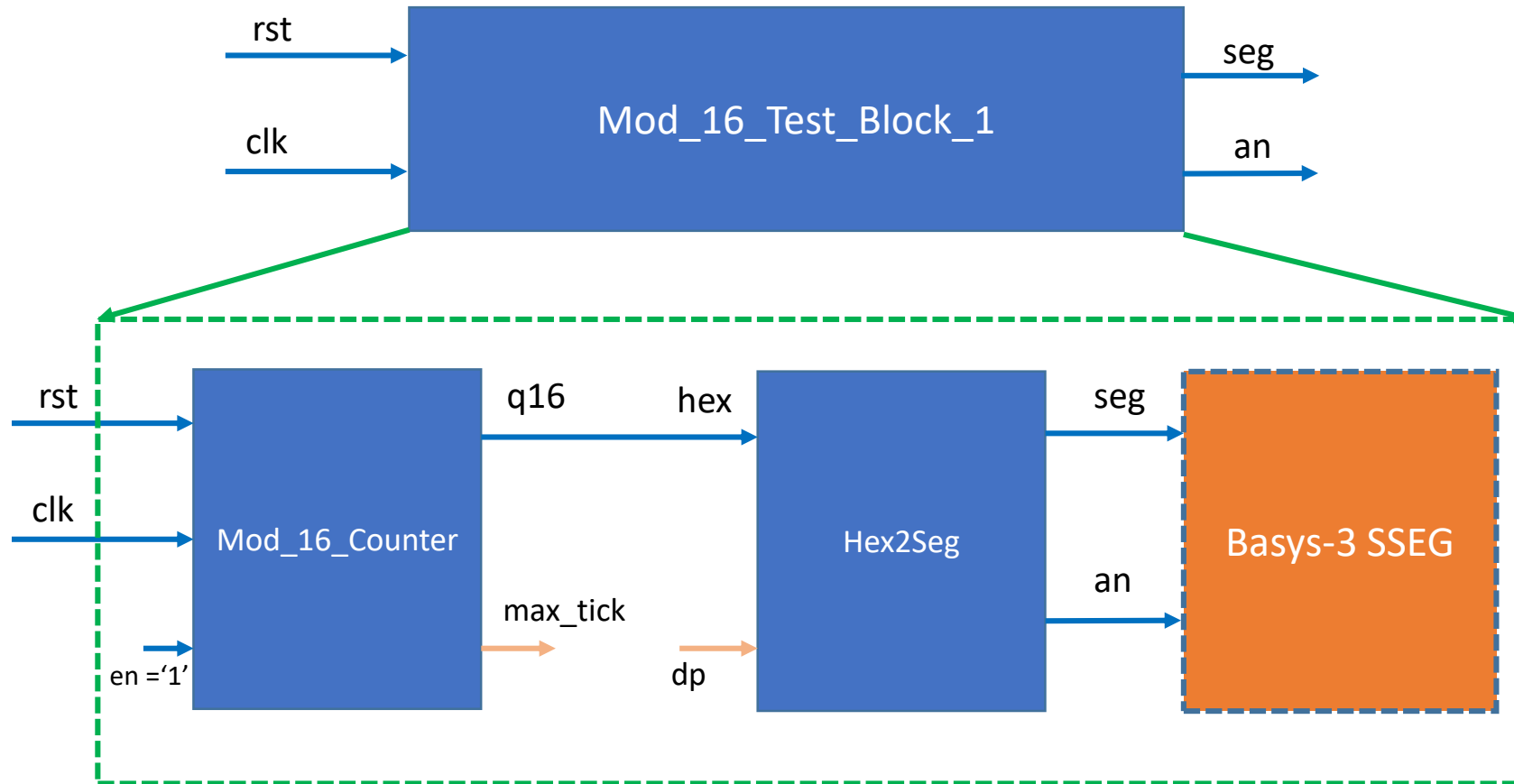


Pin Connections

Design	Basys-3
rst	btnC
clk	clk
seg	seg
an	an

Design 05: Mod-M Teller | Test

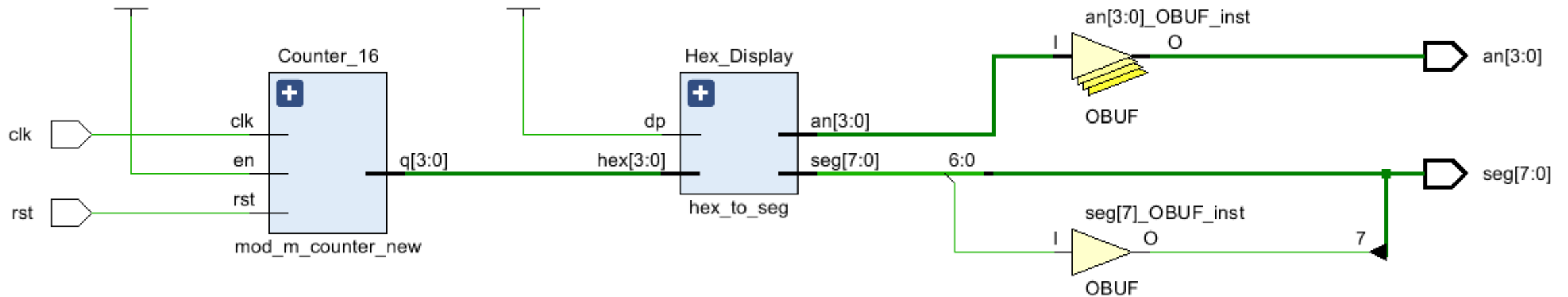

Mod-16 Counter | HardWare Testing (2)

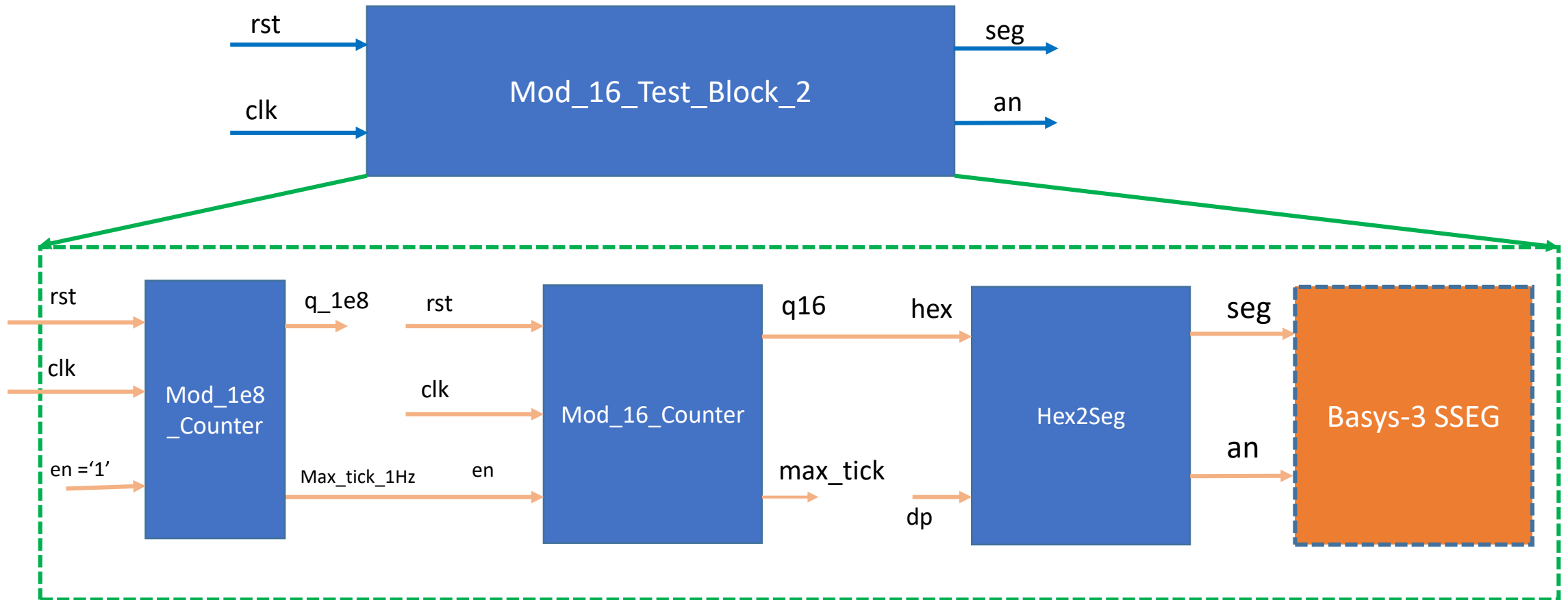

Design 05: Mod-M Teller | Test

